

Shift Registers

Shift Register Operations

Types of Shift Register Data I/Os

Serial In/Serial Out Shift Registers

Serial In/Parallel Out Shift Registers

Parallel In/Serial Out Shift Registers

Shift Register Counters

The Johnson Counter

The Ring Counter

Shift Register Applications

Time Delay

Serial-to-Parallel Data Converter

Universal Asynchronous Receiver Transmitter (UART)

Keyboard Encoder

Shift Registers

Shift Register Operations

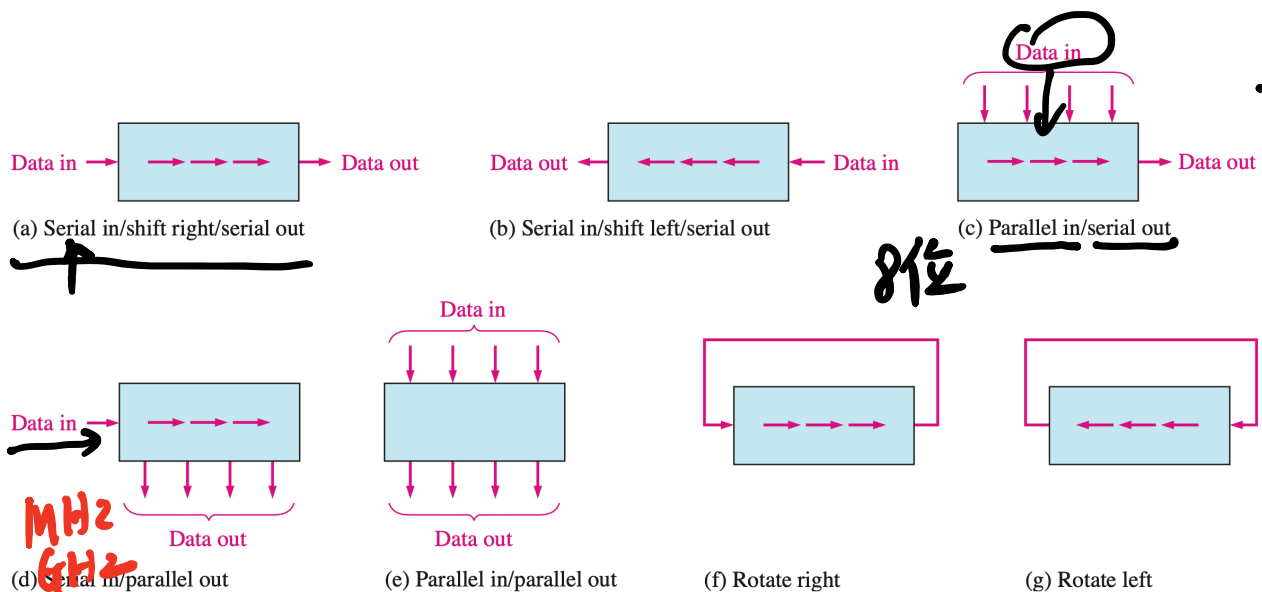


FIGURE 8-2 Basic data movement in shift registers. (Four bits are used for illustration. The bits move in the direction of the arrows.)

Types of Shift Register Data I/Os

Serial In/Serial Out Shift Registers

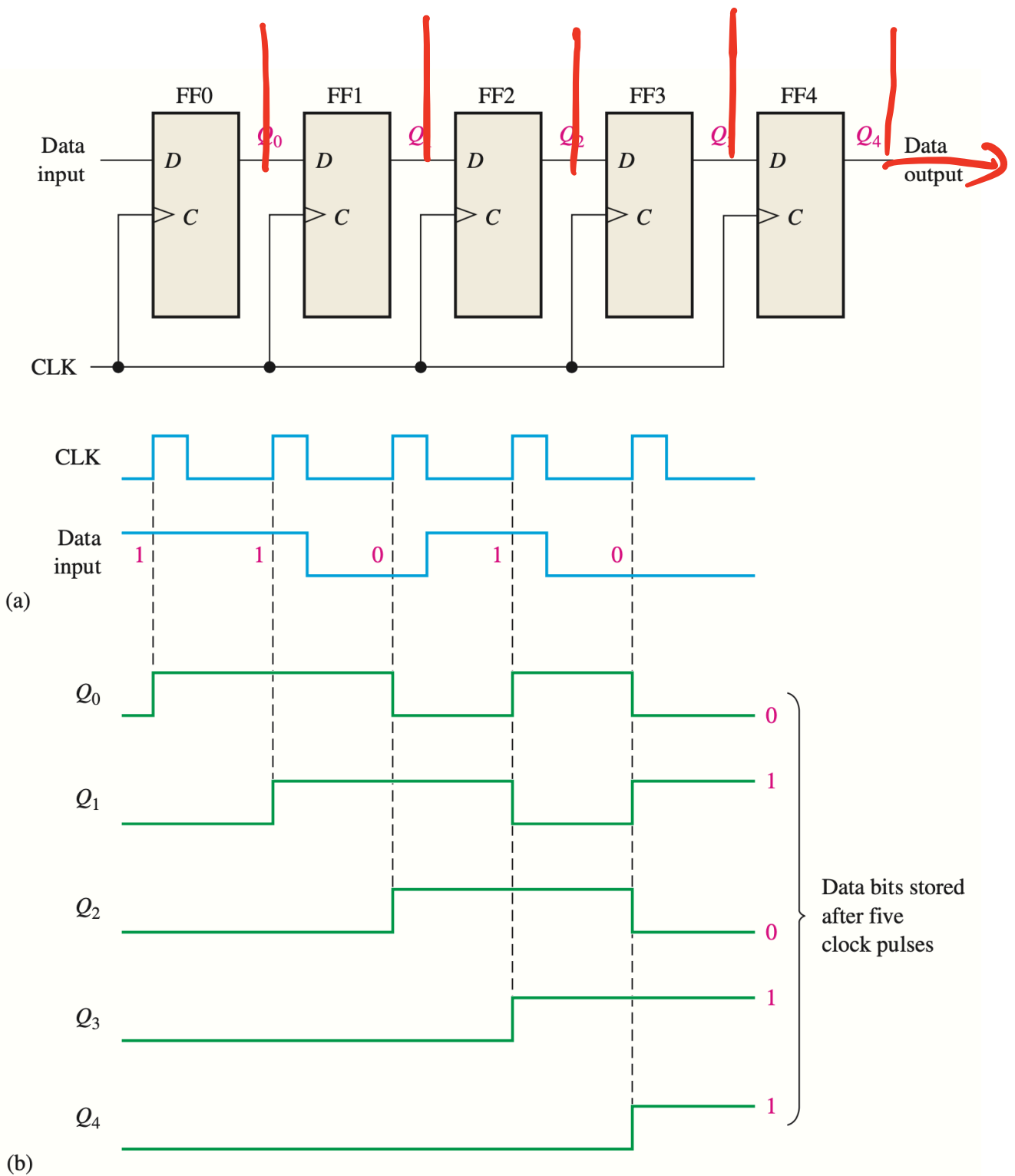


FIGURE 8-4 Open file F08-04 to verify operation. A Multisim tutorial is available on

 


FIGURE 8-5 Logic symbol for an 8-bit serial in/serial out shift register.

Serial In/Parallel Out Shift Registers

 


FIGURE 8-6 A serial in/parallel out shift register.



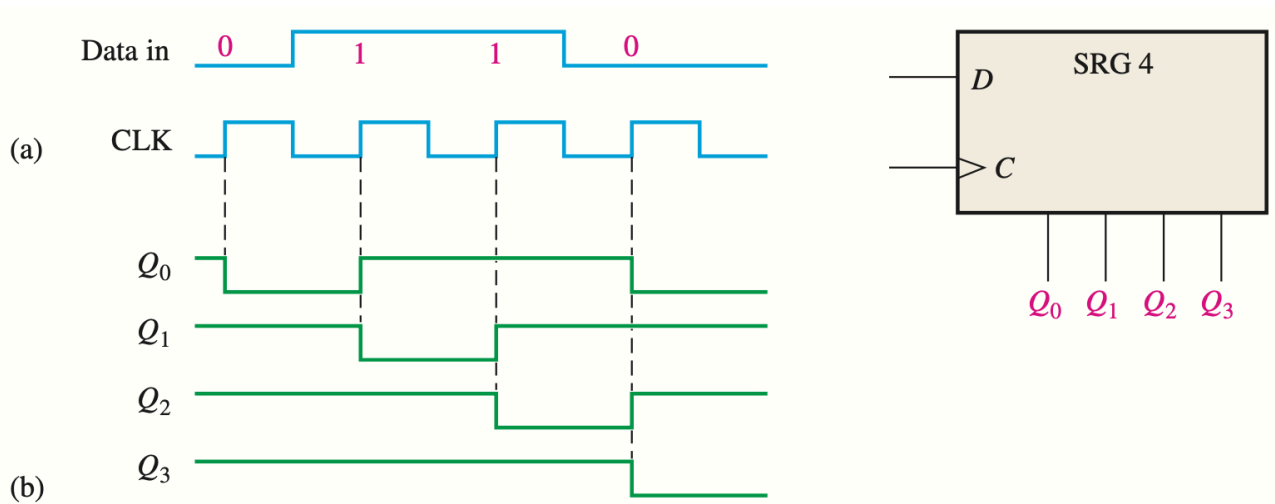


FIGURE 8-7

Parallel In/Serial Out Shift Registers

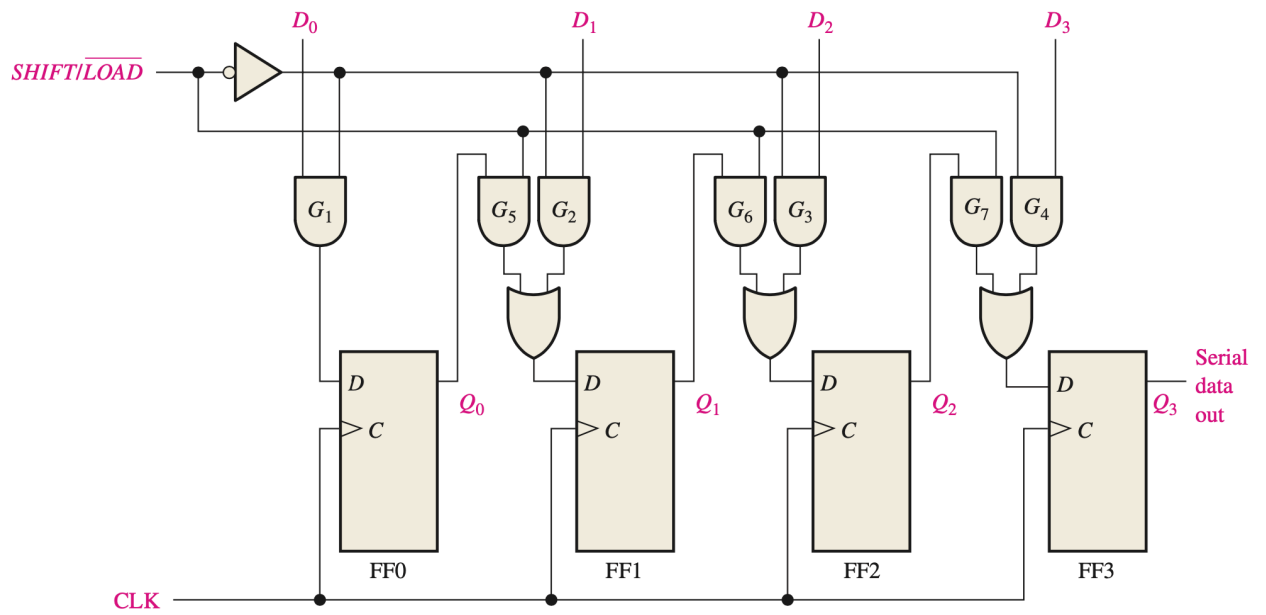

(a) Logic diagram

 

(b) Logic symbol

FIGURE 8-10 A 4-bit parallel in/serial out shift register. Open file F08-10 to verify operation.



EXAMPLE 8-3

Show the data-output waveform for a 4-bit register with the parallel input data and the clock and *SHIFT/LOAD* waveforms given in Figure 8-11(a). Refer to Figure 8-10(a) for the logic diagram.


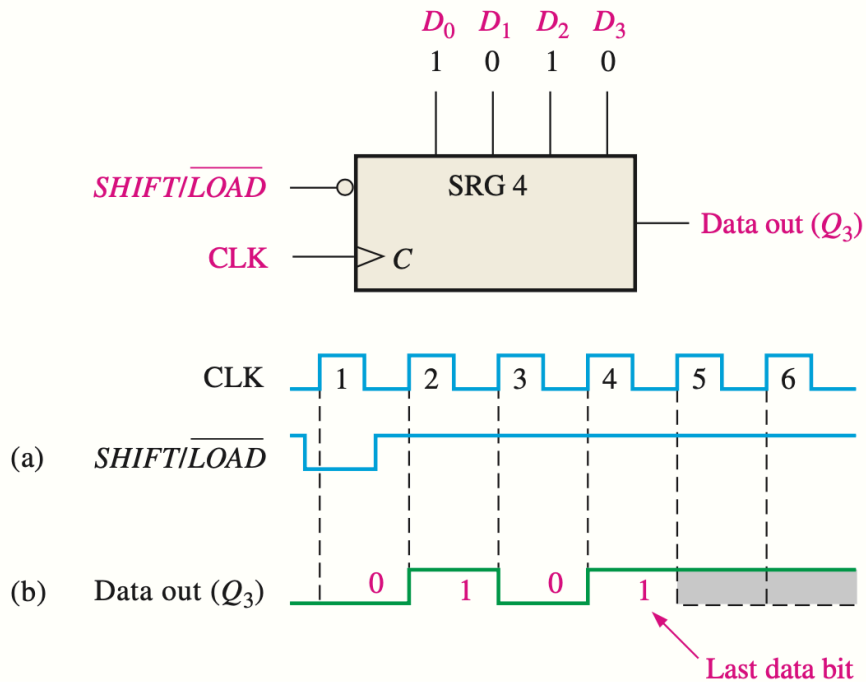



FIGURE 8-11

Shift Register Counters

The Johnson Counter

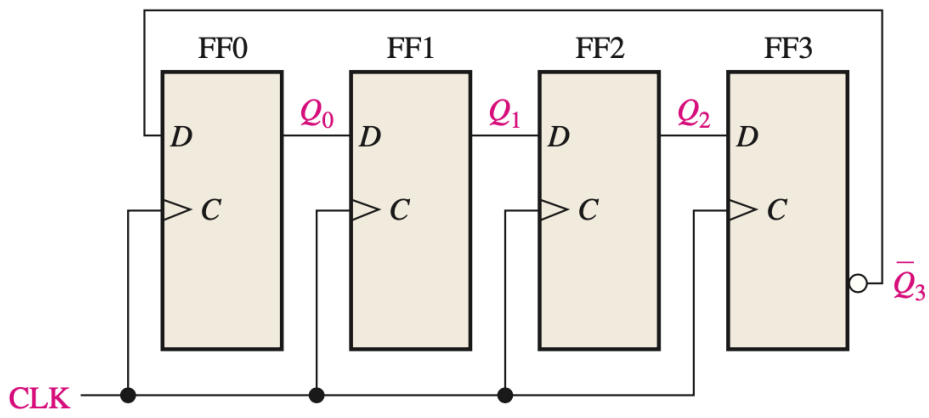


(a) Four-bit Johnson counter

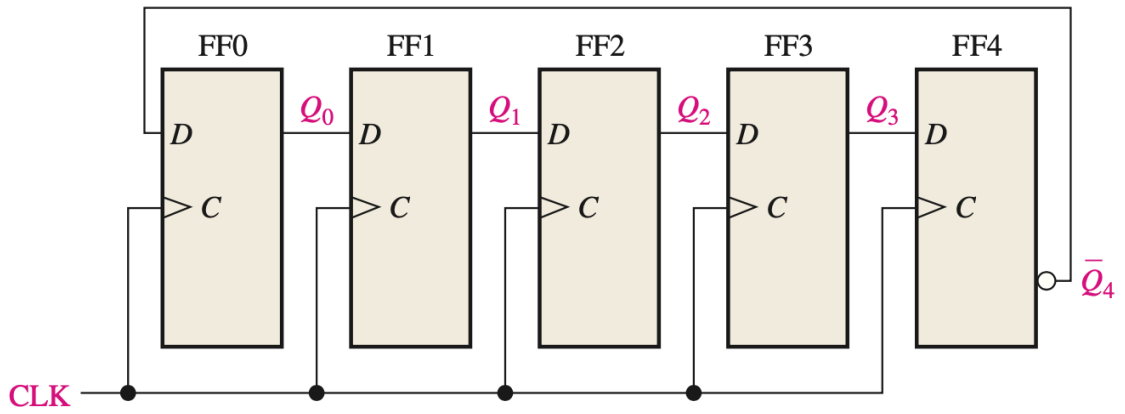



(b) Five-bit Johnson counter

FIGURE 8-21 Four-bit and 5-bit Johnson counters.


 





(a) Four-bit Johnson counter

 

 

$Q_3 Q_2 Q_1 Q_0$

  

   

 
 


TABLE 8-3

Four-bit Johnson sequence.

Clock Pulse	Q_0	Q_1	Q_2	Q_3
0	0	0	0	0
1	1	0	0	0
2	1	1	0	0
3	1	1	1	0
4	1	1	1	1
5	0	1	1	1
6	0	0	1	1
7	0	0	0	1

TABLE 8-4

Five-bit Johnson sequence.

Clock Pulse	Q_0	Q_1	Q_2	Q_3	Q_4
0	0	0	0	0	0
1	1	0	0	0	0
2	1	1	0	0	0
3	1	1	1	0	0
4	1	1	1	1	0
5	1	1	1	1	1
6	0	1	1	1	1
7	0	0	1	1	1
8	0	0	0	1	1
9	0	0	0	0	1

The Ring Counter

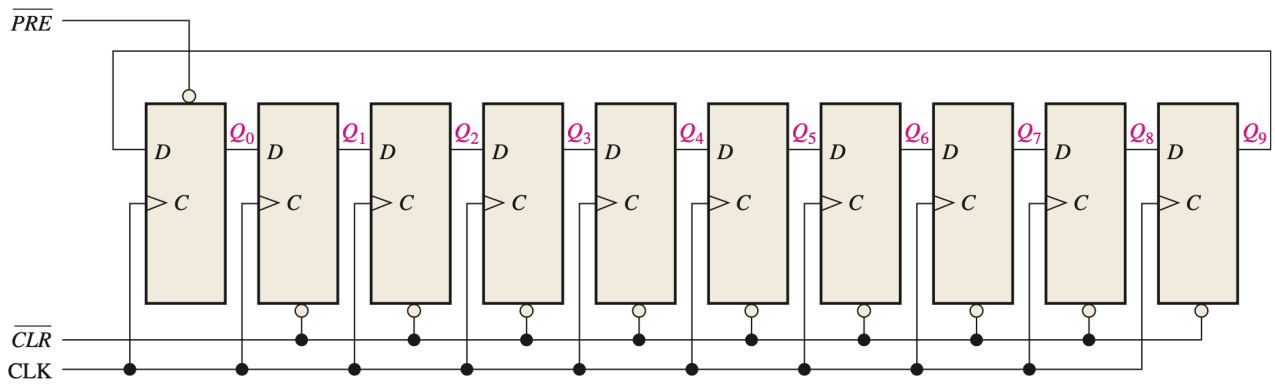


FIGURE 8-24 A 10-bit ring counter. Open file F08-24 to verify operation.

MultiSim

TABLE 8-5

Ten-bit ring counter sequence.

Clock Pulse	Q_0	Q_1	Q_2	Q_3	Q_4	Q_5	Q_6	Q_7	Q_8	Q_9
0	1	0	0	0	0	0	0	0	0	0
1	0	1	0	0	0	0	0	0	0	0
2	0	0	1	0	0	0	0	0	0	0
3	0	0	0	1	0	0	0	0	0	0
4	0	0	0	0	1	0	0	0	0	0
5	0	0	0	0	0	1	0	0	0	0
6	0	0	0	0	0	0	1	0	0	0
7	0	0	0	0	0	0	0	1	0	0
8	0	0	0	0	0	0	0	0	1	0
9	0	0	0	0	0	0	0	0	0	1

Shift Register Applications

Time Delay

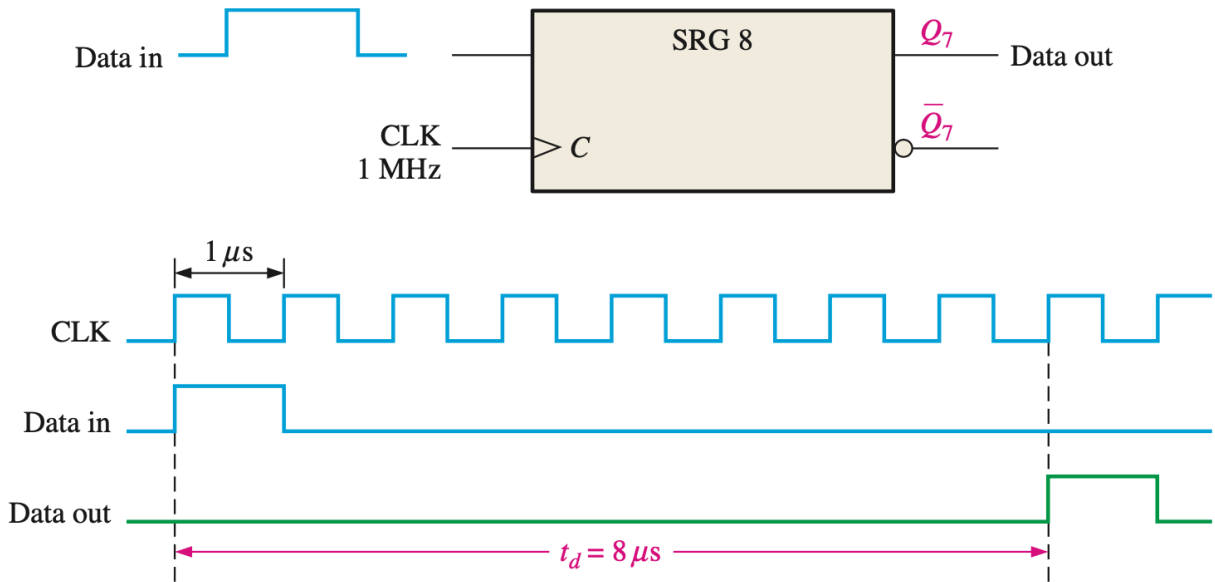


FIGURE 8-26 The shift register as a time-delay device.

Serial-to-Parallel Data Converter

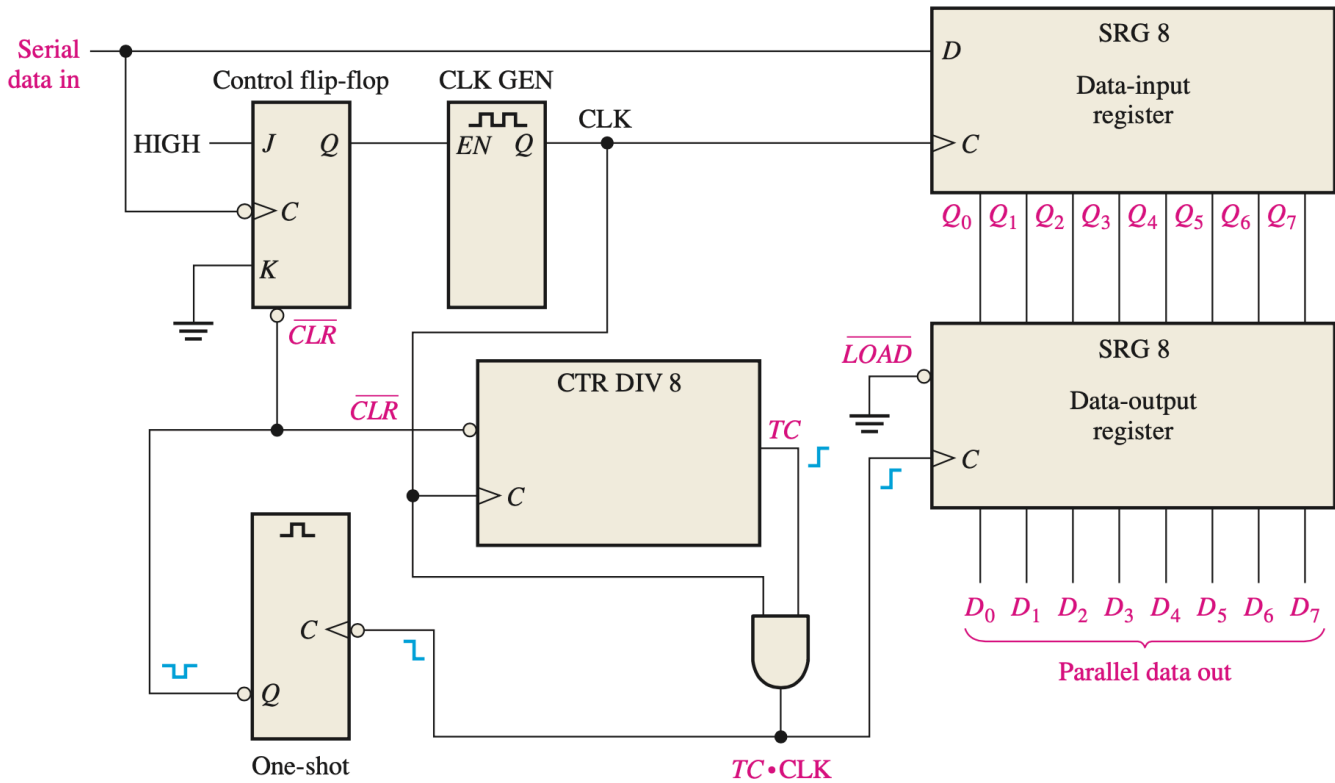


FIGURE 8-31 Simplified logic diagram of a serial-to-parallel converter.

Universal Asynchronous Receiver Transmitter (UART)

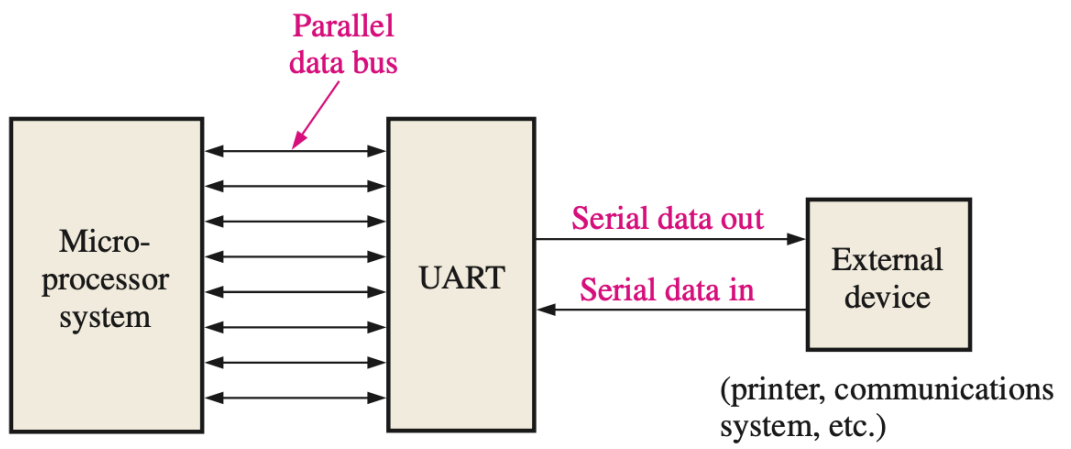


FIGURE 8-34 UART interface.

Keyboard Encoder

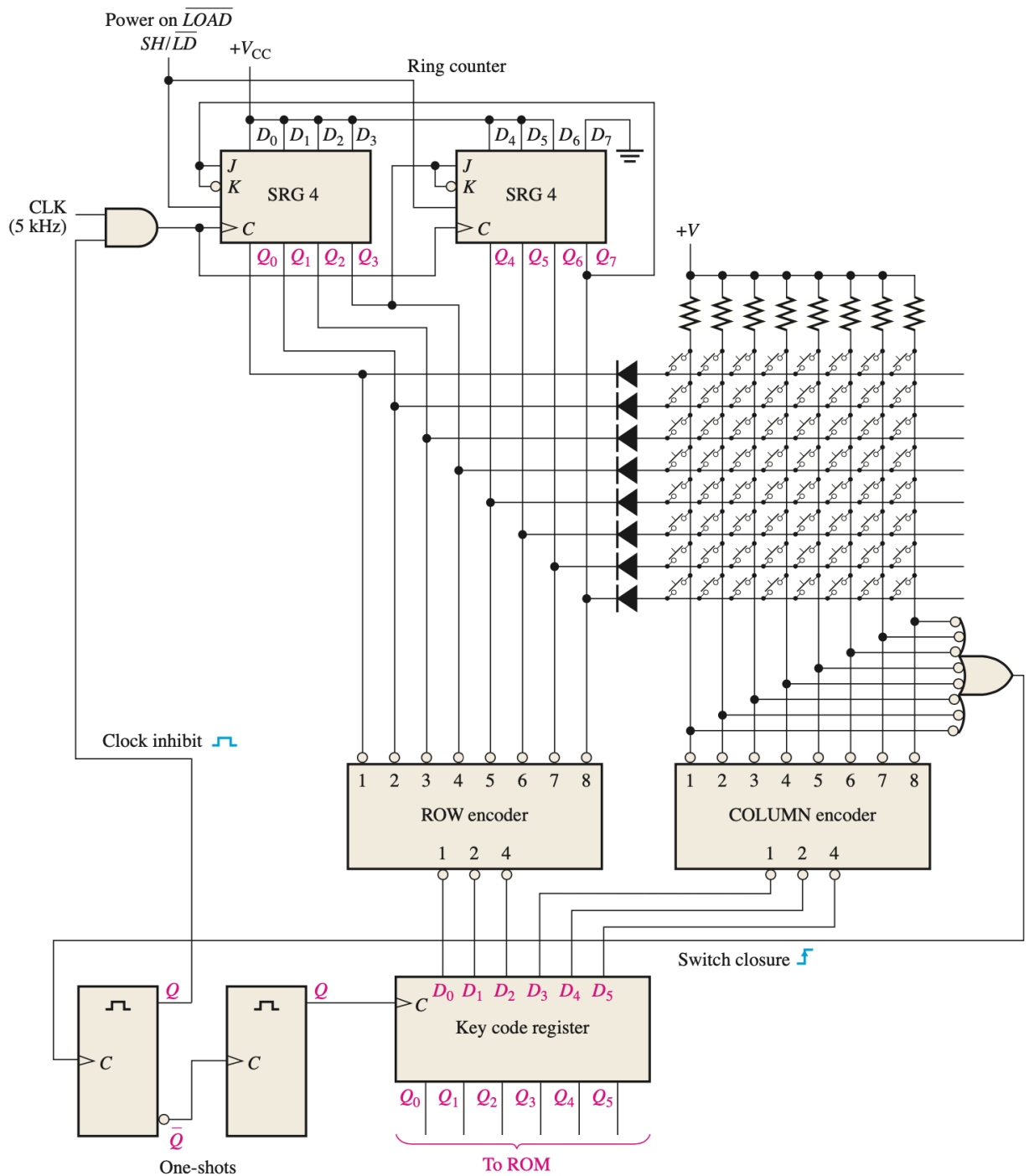


FIGURE 8-36 Simplified keyboard encoding circuit.