
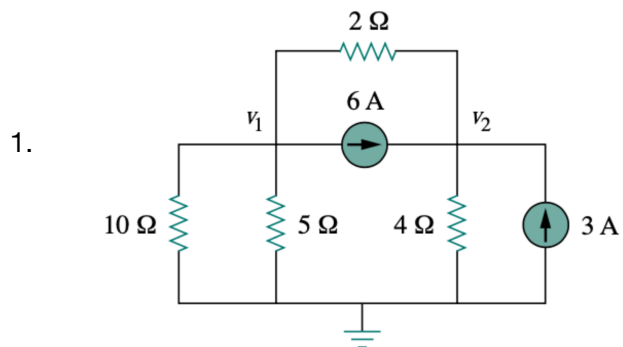


Chap3

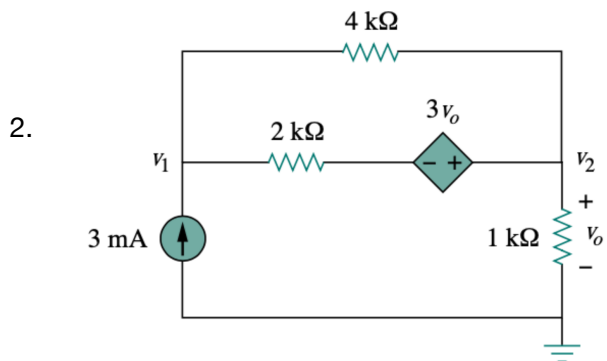
For the circuit in Fig. 3.51, obtain v_1 and v_2 .



For the circuit in Fig. 3.66, find v_1 and v_2 using nodal analysis.



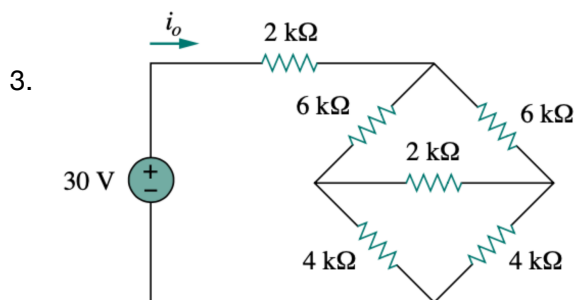For the bridge network in Fig. 3.76, find i_o using mesh analysis.



Find v_x and i_x in the circuit shown in Fig. 3.91.

