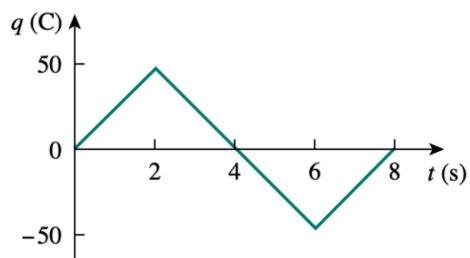


The charge flowing in a wire is plotted in Fig. 1.21. Sketch the corresponding current.



- 1.12** The current entering the positive terminal of a device is  $i(t) = 3e^{-2t}$  A and the voltage across the device is  $v(t) = 5 \, di/dt$  V.
- (a) Find the charge delivered to the device between  $t = 0$  and  $t = 2$  s.
  - (b) Calculate the power absorbed.
  - (c) Determine the energy absorbed in 3 s.

- 1.15** Find the power absorbed by each of the elements in Fig. 1.26.

