
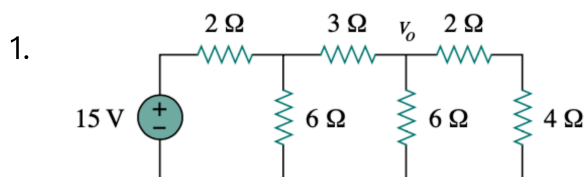


Chap4

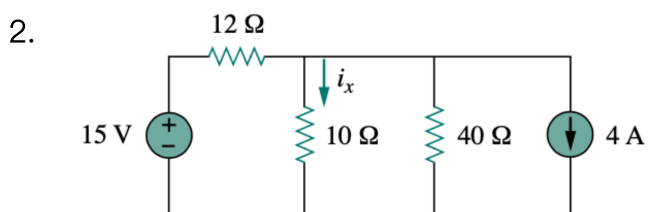
For the circuit in Fig. 4.73, assume $v_o = 1$ V, and use linearity to find the actual value of v_o .




Given the circuit in Fig. 4.75, calculate i_x and the power dissipated by the $10\text{-}\Omega$ resistor using superposition.




Find v_x in Fig. 4.83 by superposition.

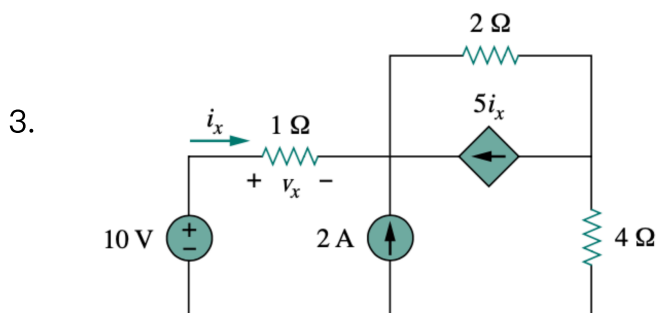

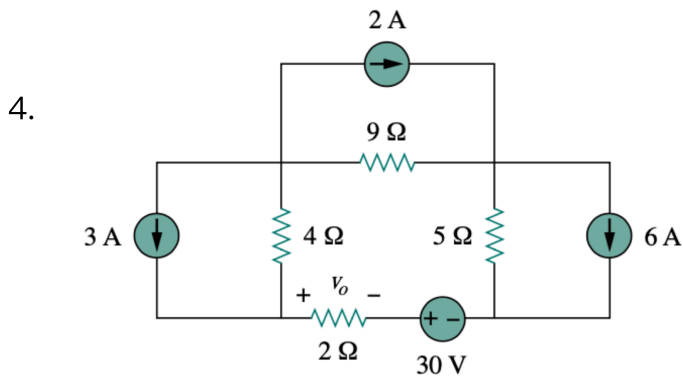
Obtain v_o in the circuit of Fig. 4.87 using source transformation. Check your result using *PSpice*.



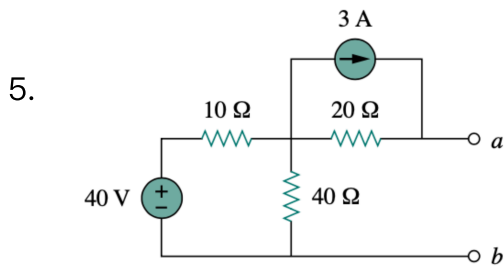Find the Thevenin equivalent at terminals a - b of the circuit in Fig. 4.93.



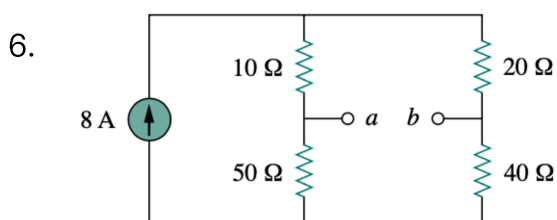Determine the Thevenin and Norton equivalents at terminals a - b of the circuit in Fig. 4.107.



For the circuit in Fig. 4.117, what resistor connected across terminals a - b will absorb maximum power from the circuit? What is that power?

