
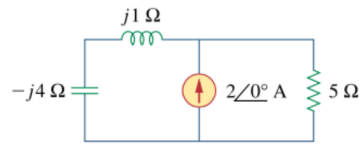


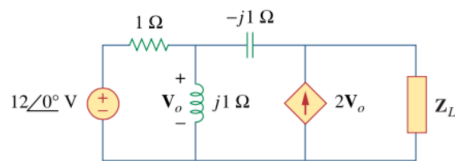Given the circuit in Fig. 11.35, find the average power supplied or absorbed by each element.




1.

In the circuit of Fig. 11.46, find the value of Z_L that will absorb the maximum power and the value of the maximum power.



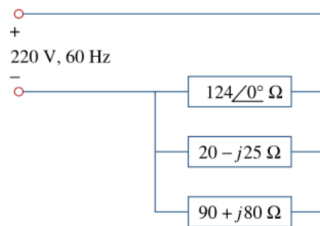2.


For the power system in Fig. 11.67, find: (a) the average power, (b) the reactive power, (c) the power factor. Note that 220 V is an rms value.



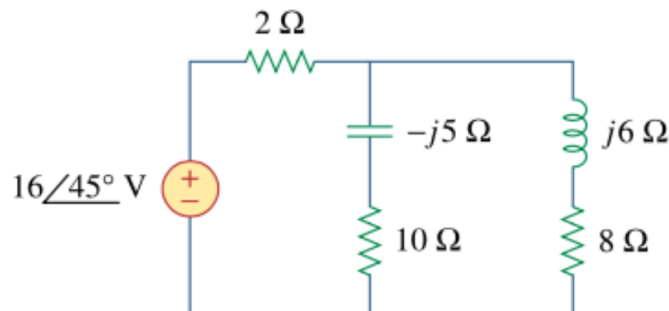3.

For the entire circuit in Fig. 11.70, calculate:

- the power factor
- the average power delivered by the source
- the reactive power
- the apparent power
- the complex power



4.