
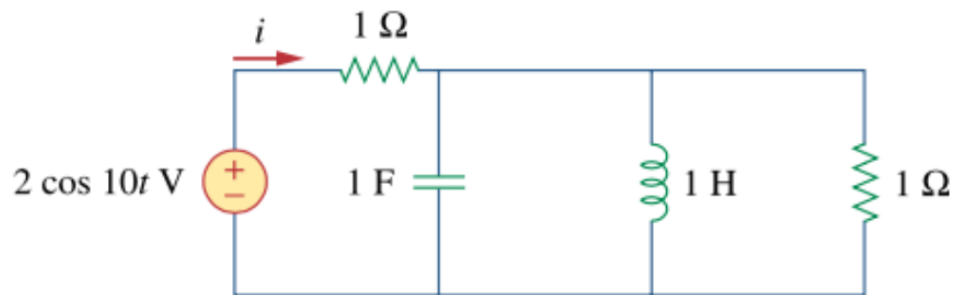


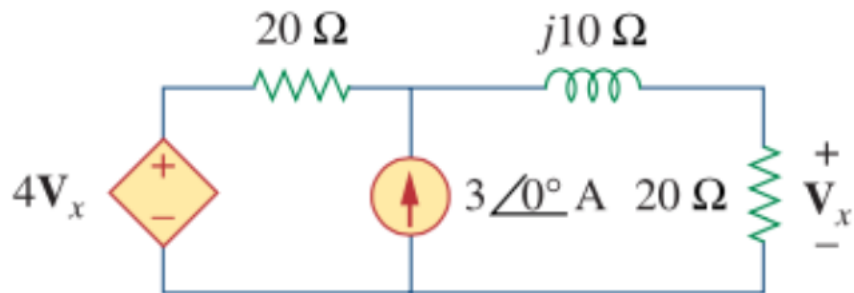
Determine i in the circuit of Fig. 10.50.




Determine V_x in Fig. 10.55.



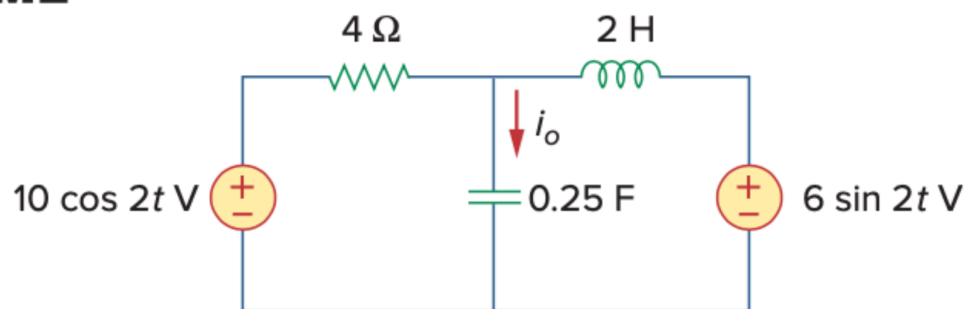10.25 Solve for i_o in Fig. 10.73 using mesh analysis.




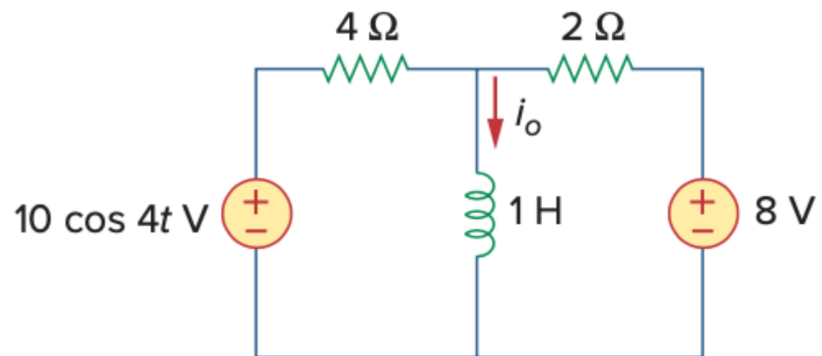10.40 Find i_o in the circuit shown in Fig. 10.85 using superposition.




4.

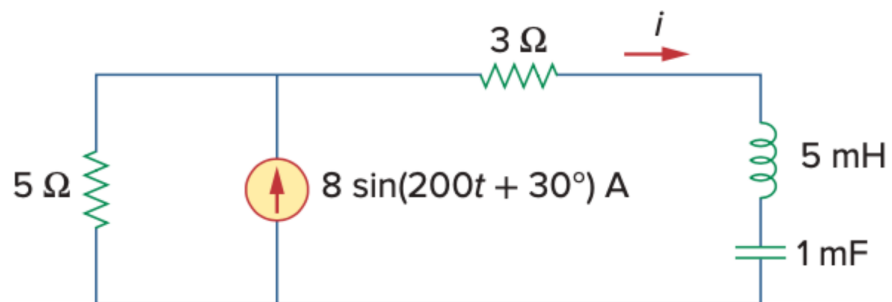10.49 Using source transformation, find i in the circuit of Fig. 10.94.




5.

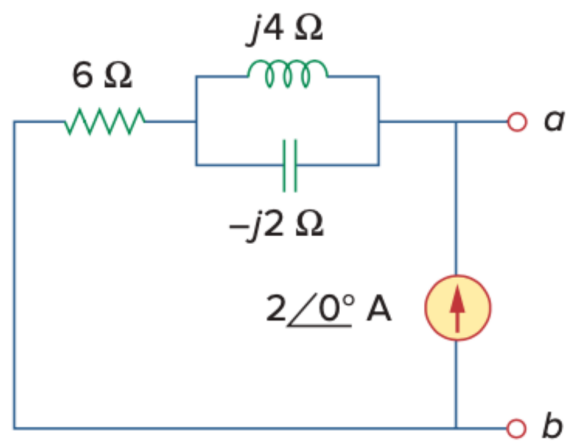10.56 For each of the circuits in Fig. 10.99, obtain Thevenin and Norton equivalent circuits at terminals a - b .



(a)

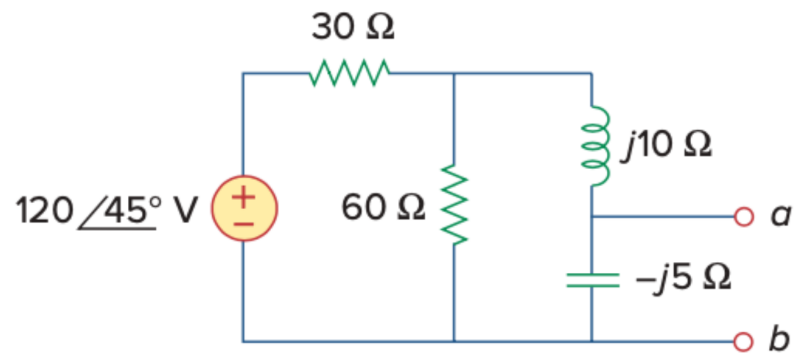

(b)