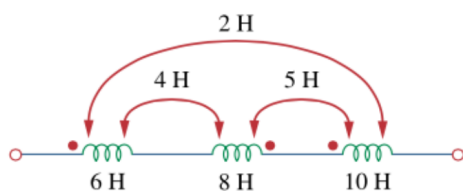


For the three coupled coils in Fig. 13.72, calculate the total inductance.




1.

13.4 (a) For the coupled coils in Fig. 13.74(a), show that


$$L_{\text{eq}} = L_1 + L_2 + 2M$$

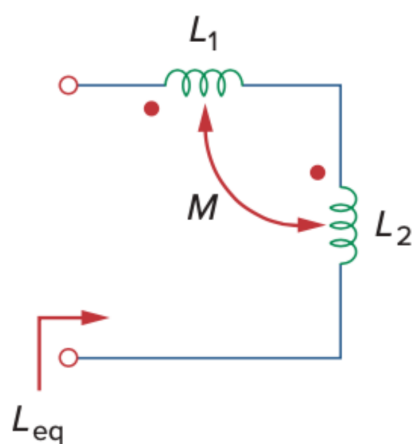(b) For the coupled coils in Fig. 13.74(b), show that

$$L_{\text{eq}} = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M}$$



(a)

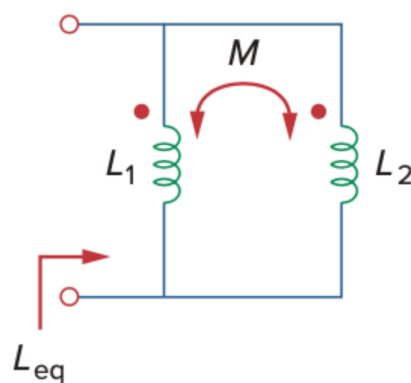


(b)

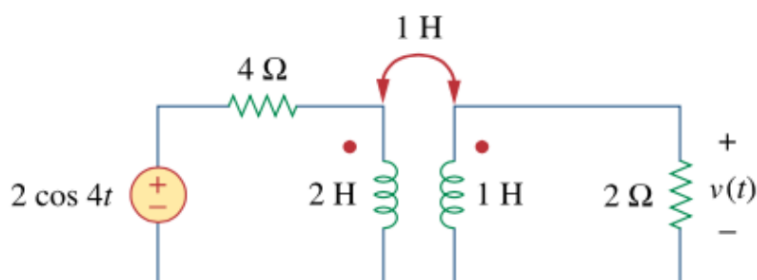2.

Chapter 13, Problem 8.




Find $v(t)$ for the circuit in Fig. 13.77.



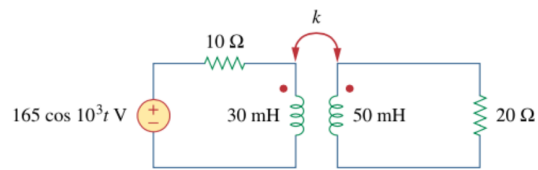
3.

In the circuit of Fig. 13.98, find the value of the coupling coefficient k that will make the $10\text{-}\Omega$ resistor dissipate 320 W . For this value of k , find the energy stored in the coupled coils at $t = 1.5\text{ s}$.



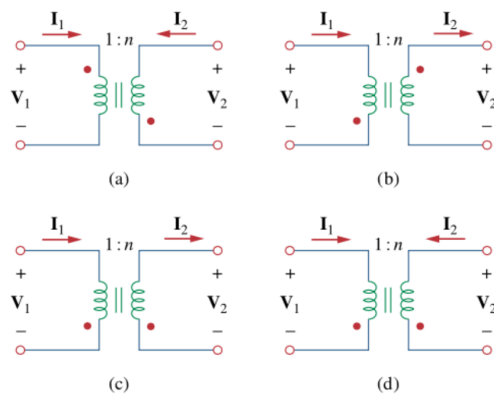4.


As done in Fig. 13.32, obtain the relationships between terminal voltages and currents for each of the ideal transformers in Fig. 13.105.



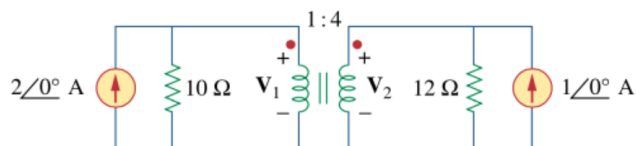5.



PS ML Obtain V_1 and V_2 in the ideal transformer circuit of Fig. 13.108.



6.